

Tips about using a multi-range ammeter


An ammeter can be used to measure the size of a current in a circuit.




Circuit symbol for ammeter



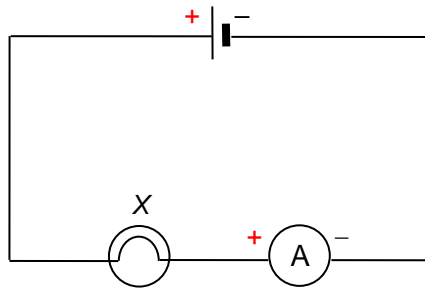An ammeter should be connected in a chain with a circuit component to measure the current passing through it. The following figures show two examples.



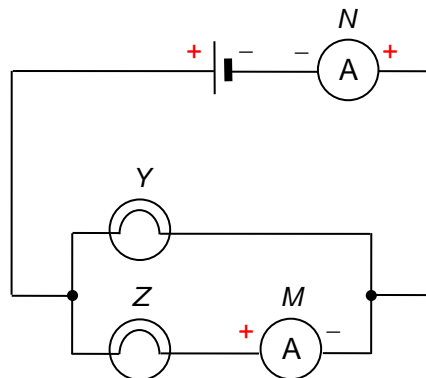The ammeter measures the current passing through bulb X (or the battery).A





Ammeter M measures the current passing through bulb Z.
Ammeter N measures the current passing through the battery.

Tips about using a multi-range ammeter


Precautions:

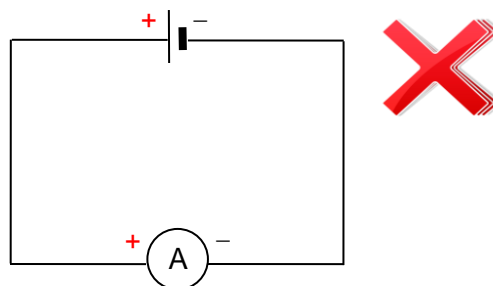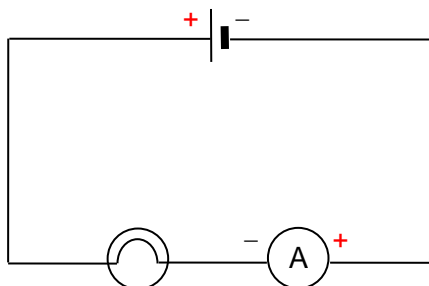- 1 The red terminal (+ terminal) of an ammeter should lead to the + terminal of the power source, and the black terminal (– terminal) to the – terminal.
- 2 An ammeter should not be connected across a source directly when there is no other component in the circuit.





The ammeters could be damaged!

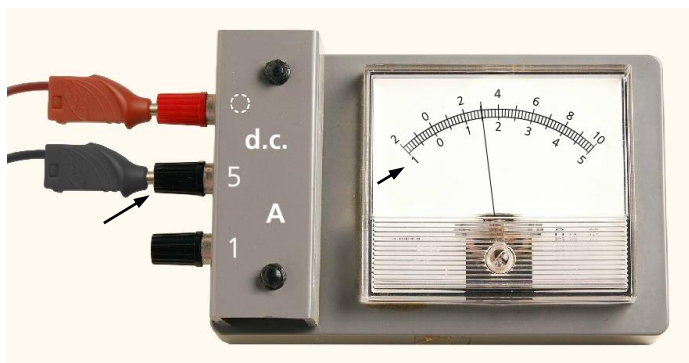- 3 Some ammeters have more than one red/black terminal for different ranges of measurements.




When the 5-A terminal is connected, maximum reading = 5 A

∴ We use the lower scale:

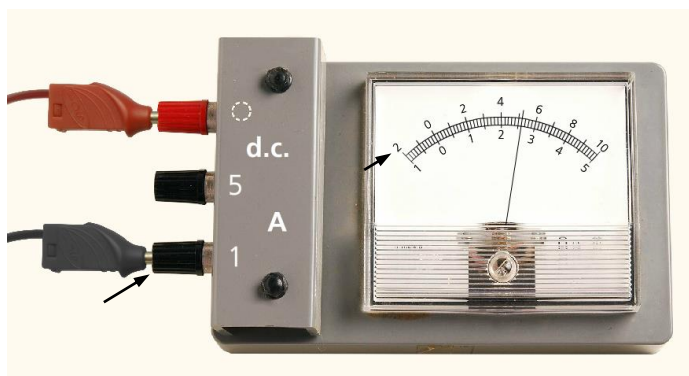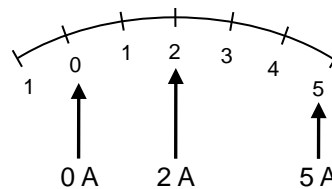

When the 1-A terminal is connected, maximum reading = 1 A

∴ We use the upper scale:

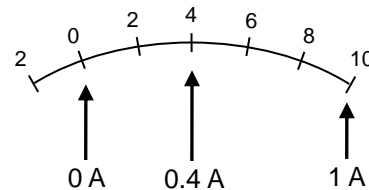


- 4 If an ammeter has multiple ranges of measurements, always use the largest range first. Switch to a smaller range for a more accurate reading only if the current measured is within that range. This avoids damaging the ammeter.


Exercise

- 1 Determine in each of the following cases whether the ammeter is properly connected to measure the current passing through bulb X. If not, give one modification to make it usable.

(a)

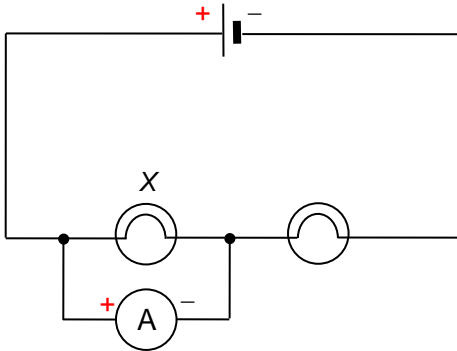


(b)

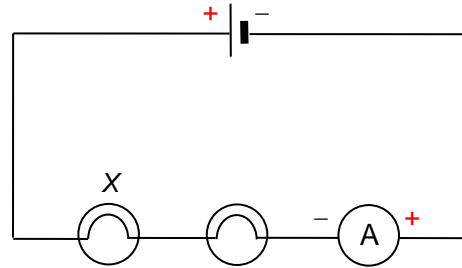


- 2 Read the ammeters in the following cases.

(a)

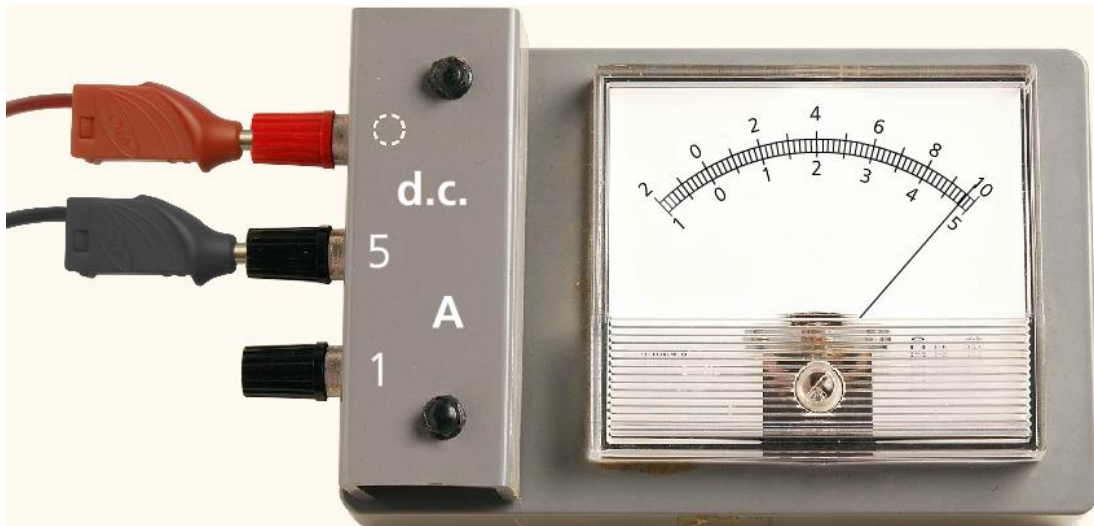

(b)

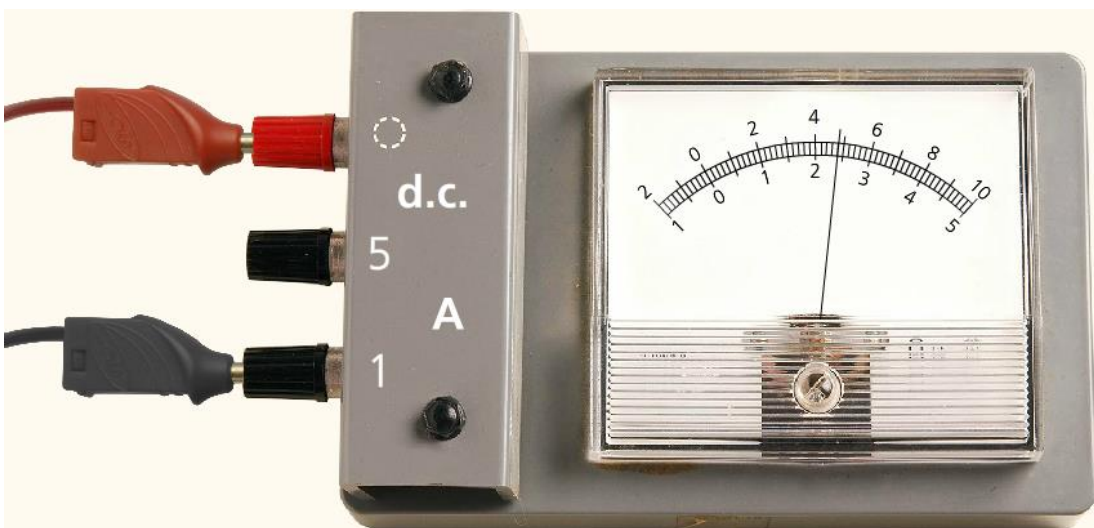

Answers

- 1 (a) No, the ammeter should be connected in a chain with bulb X.
(b) No, the connections to the positive and negative terminals of the ammeter should be interchanged.
- 2 (a) 4.8 A
(b) 0.48 A